

# 组合电路的门电路实现

**例：习题2.12** 举重比赛有3个裁判，一个是主裁判A，另外两个是副裁判B和C。运动员一次举重是否成功，由裁判员各自按动他面前的按钮决定，只有两个以上（其中必须有主裁判）判定为成功，表示“成功”的灯泡L才亮。试列出真值表和逻辑表达式。


真值表

A	B	C	L
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


逻辑表达式：

$$L = A\bar{B}C + AB\bar{C} + ABC$$
$$= AC + AB$$

逻辑电路：

 


## 用逻辑门设计组合电路的过程

 

# 例1 设计一个4线—2线编码器

框图

 


功能表

x <sub>3</sub>	x <sub>2</sub>	x <sub>1</sub>	x <sub>0</sub>	b <sub>1</sub>	b <sub>0</sub>
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
其 它				?	?

怎么办  
? 能为  
任意X?

改进框图

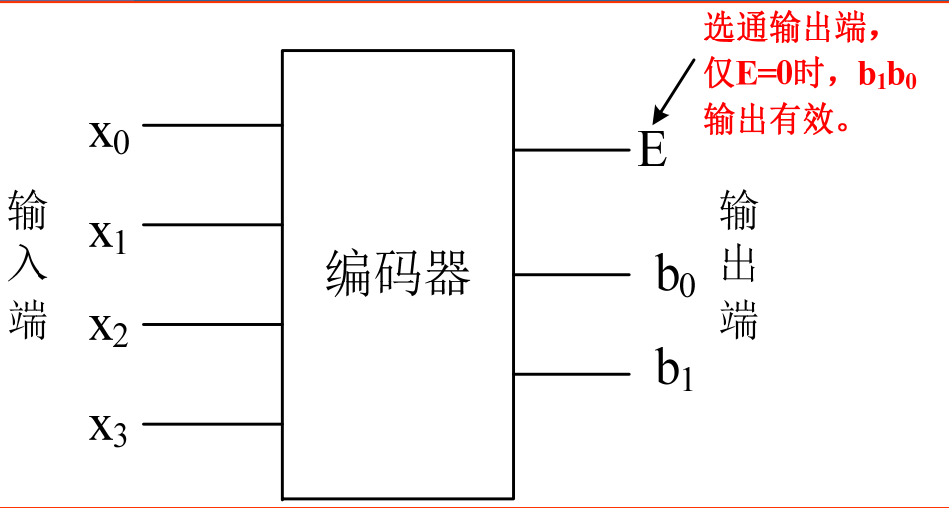


新的功能表

x <sub>3</sub>	x <sub>2</sub>	x <sub>1</sub>	x <sub>0</sub>	E	b <sub>1</sub>	b <sub>0</sub>
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	1	0
1	0	0	0	0	1	1
其 它				1	X	X

E=1, b<sub>1</sub>b<sub>0</sub>输出无  
意义 (即无效)

如果

 


功能表

$a_3$	$a_2$	$a_1$	$a_0$	E	$b_1$	$b_0$
1	1	1	0	0	0	0
1	1	0	1	0	0	1
1	0	1	1	0	1	0
0	1	1	1	0	1	1
其它				1	X	X

输入低电平有效

注意：书上按键方向画反了

电路图

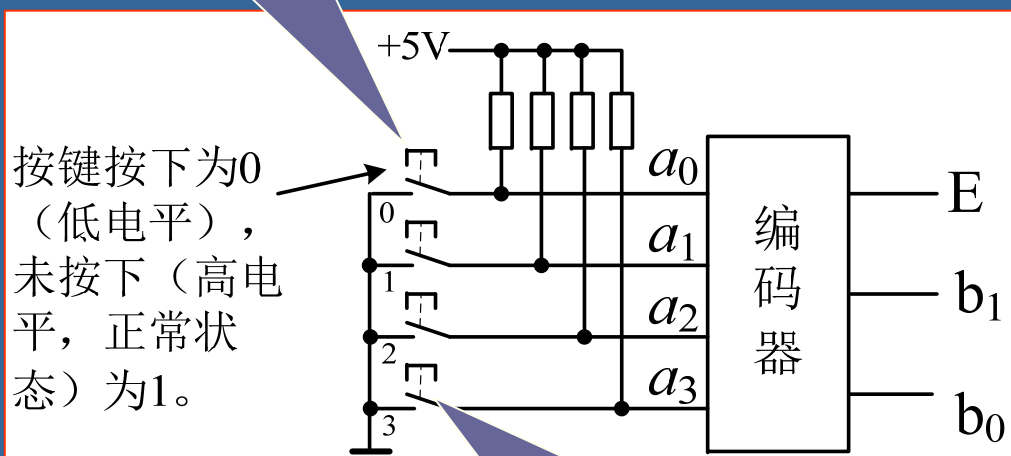


现在问题是：如何同时按下多个按键怎么办？

答案是采用优先级，即所谓的优先编码。

$a_3$	$a_2$	$a_1$	$a_0$	E	$b_1$	$b_0$
1	1	1	0	0	0	0
1	1	0	X	0	0	1
1	0	X	X	0	1	0
0	X	X	X	0	1	1
1	1	1	1	1	X	X

优先编码， $a_3$  的权限最高， $a_0$  的权限最低

X表示任意，即 无论是0还是1

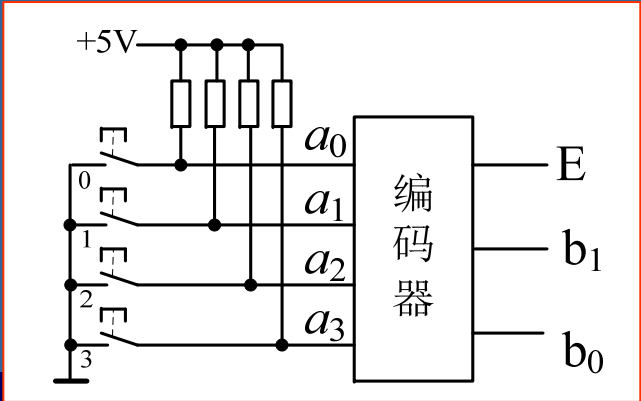

若交换一下行的上下顺序

$a_3$	$a_2$	$a_1$	$a_0$	E	$b_1$	$b_0$
1	1	1	1	1	X	X
0	X	X	X	0	1	1
1	0	X	X	0	1	0
1	1	0	X	0	0	1
1	1	1	0	0	0	0

这个就是教材 P89 表3-2-1 4 线—2线优先编码器功能表

$a_3$	$a_2$	$a_1$	$a_0$	E	$b_1$	$b_0$
1	1	1	1	1	X	X
0	X	X	X	0	1	1
1	0	X	X	0	1	0
1	1	0	X	0	0	1
1	1	1	0	0	0	0

$a_1 a_0$		$a_3 a_2$			
		00	01	11	10
00	00	011	011	011	011
01	01	011	011	011	011
11	11	001	001	1xx	000
10	10	010	010	010	010

$Eb_1b_0$

$a_1 a_0$		$a_3 a_2$			
		00	01	11	10
00	00	0	0	0	0
01	01	0	0	0	0
11	11	0	0	1	0
10	10	0	0	0	0

$E$

$a_1 a_0$		$a_3 a_2$			
		00	01	11	10
00	00	1	1	1	1
01	01	1	1	1	1
11	11	0	0	x	0
10	10	1	1	1	1

$b_1$

$a_1 a_0$		$a_3 a_2$			
		00	01	11	10
00	00	1	1	1	1
01	01	1	1	1	1
11	11	1	1	x	0
10	10	0	0	0	0

$b_0$

$$E = a_3 a_2 a_1 a_0$$

$$b_1 = \bar{a}_3 + \bar{a}_2$$

$$b_0 = \bar{a}_3 + a_2 \bar{a}_1$$


$$E = a_3 a_2 a_1 a_0$$

逻辑表达式:

$$b_1 = \bar{a}_3 + \bar{a}_2$$


$$b_0 = \bar{a}_3 + a_2 \bar{a}_1$$

逻辑电路图:

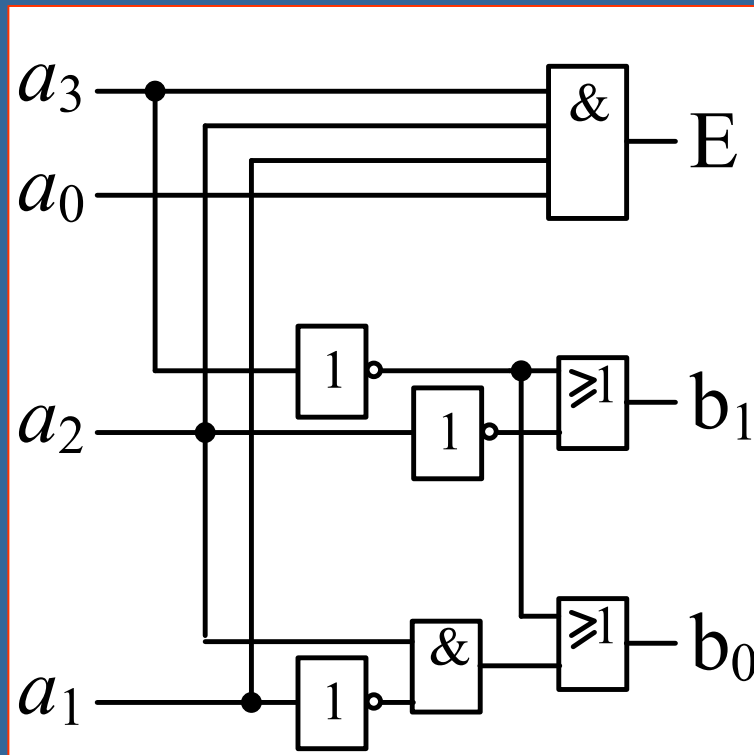

4线—2线优先编码器

## 例2 设计一个2线—4线译码器 框 图

 

### 真值表

行号	$b_1$	$b_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	1
1	0	1	0	0	1	0
2	1	0	0	1	0	0
3	1	1	1	0	0	0


### 逻辑表达式

$$Y_3 = b_1 b_0 = m_3 \quad Y_2 = b_1 \bar{b}_0 = m_2$$

$$Y_1 = \bar{b}_1 b_0 = m_1 \quad Y_0 = \bar{b}_1 \bar{b}_0 = m_0$$


译码是编码的逆过程，在编码时，每一种二进制代码，都赋予了特定的含义，即都表示了一个确定的信号或者对象。把代码状态的特定含义“翻译”出来的过程叫做译码，实现译码操作的电路称为译码器。也就是说，译码器是可以将输入二进制代码的状态翻译成输出信号，以表示其原来含义的电路。

### 逻辑图

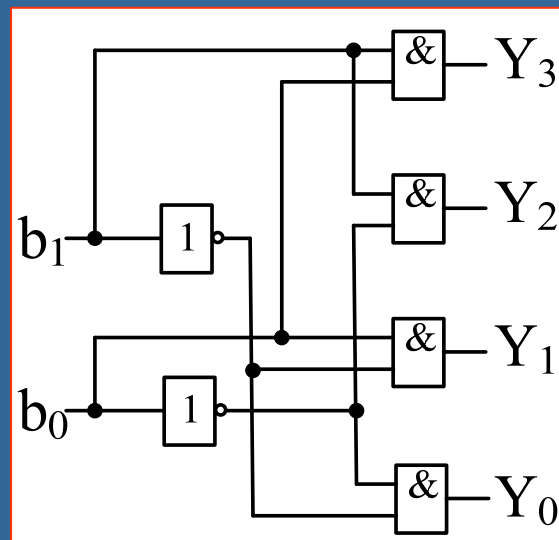


### 例3 设计一个2位并行加法器

#### 框图

 

根据加法的运算性质，可以分解成两个1位加法器级联而成。

 

#### 逻辑表达式

$$\Sigma_0 = a_0 \oplus b_0 \oplus CI_0$$

$$\Sigma_1 = a_1 \oplus b_1 \oplus CI_1$$

$$CI_1 = a_0 b_0 + a_0 CI_0 + b_0 CI_0$$

$$CO = a_1 b_1 + a_1 CI_1 + b_1 CI_1$$

但该电路有一个明显的缺点，即只有等  $CI_1$  产生后，才能有  $CO$ 。对于多级电路来说，这样会大大地影响电路运行速度。



逻辑表达式  $\Sigma_0 = a_0 \oplus b_0 \oplus CI_0$

$$\Sigma_1 = a_1 \oplus b_1 \oplus CI_1$$

$$CI_1 = a_0 b_0 + a_0 CI_0 + b_0 CI_0$$

$$CO = a_1 b_1 + a_1 CI_1 + b_1 CI_1$$

令  $G_0 = a_0 b_0, \quad P_0 = a_0 + b_0$

$$G_1 = a_1 b_1, \quad P_1 = a_1 + b_1$$

则  $\because P_0 \cdot \overline{G}_0 = (a_0 + b_0) \cdot \overline{a_0 b_0} = (a_0 + b_0)(\overline{a_0} + \overline{b_0})$   
 $= a_0 \overline{b_0} + \overline{a_0} b_0 = a_0 \oplus b_0$

$$\therefore \Sigma_0 = a_0 \oplus b_0 \oplus CI_0 = (P_0 \cdot \overline{G}_0) \oplus CI_0$$

同理  $\Sigma_1 = a_1 \oplus b_1 \oplus CI_1 = (P_1 \cdot \overline{G}_1) \oplus CI_1$

$$\begin{aligned}
 CI_1 &= a_0 b_0 + a_0 CI_0 + b_0 CI_0 = a_0 b_0 + CI_0 (a_0 + b_0) \\
 &= G_0 + CI_0 P_0 = \overline{\overline{G_0 + CI_0 P_0}} \\
 &= \overline{\overline{G_0} (\overline{CI_0} + \overline{P_0})} = \overline{\overline{G_0} \overline{P_0} + \overline{G_0} \overline{CI_0}}
 \end{aligned}$$

$$\begin{aligned}
 \therefore \overline{\overline{G_0} \overline{P_0}} &= \overline{a_0 b_0 \cdot (a_0 + b_0)} = \overline{(\overline{a_0} + \overline{b_0}) \overline{a_0} \overline{b_0}} \\
 &= \overline{\overline{a_0} + \overline{b_0}} = \overline{P_0}
 \end{aligned}$$

$$\therefore CI_1 = \overline{\overline{P_0} + \overline{G_0} \overline{CI_0}}$$

$$CO = a_1 b_1 + a_1 CI_1 + b_1 CI_1 = a_1 b_1 + CI_1(a_1 + b_1)$$

$$= G_1 + CI_1 P_1 = \overline{\overline{G_1 + CI_1 P_1}}$$

$$= \overline{\overline{G_1} \overline{P_1} + \overline{G_1} \overline{CI_1}} = \overline{\overline{P_1} + \overline{G_1} \overline{CI_1}}$$

$$= \overline{\overline{P_1} + \overline{G_1} \overline{G_0} (\overline{CI_0} + \overline{P_0})}$$

$$= \overline{\overline{P_1} + \overline{P_0} \overline{G_1} + \overline{G_0} \overline{G_1} \overline{CI_0}}$$


## 变换后的逻辑表达式

$$\Sigma_0 = (P_0 \cdot \bar{G}_0) \oplus CI_0 \quad \Sigma_1 = (P_1 \cdot \bar{G}_1) \oplus CI_1$$

$$CI_1 = \bar{P}_0 + \bar{G}_0 \bar{CI}_0$$

$$CO = \bar{P}_1 + \bar{P}_0 \bar{G}_1 + \bar{G}_0 \bar{G}_1 \bar{CI}_0$$

## 逻辑图

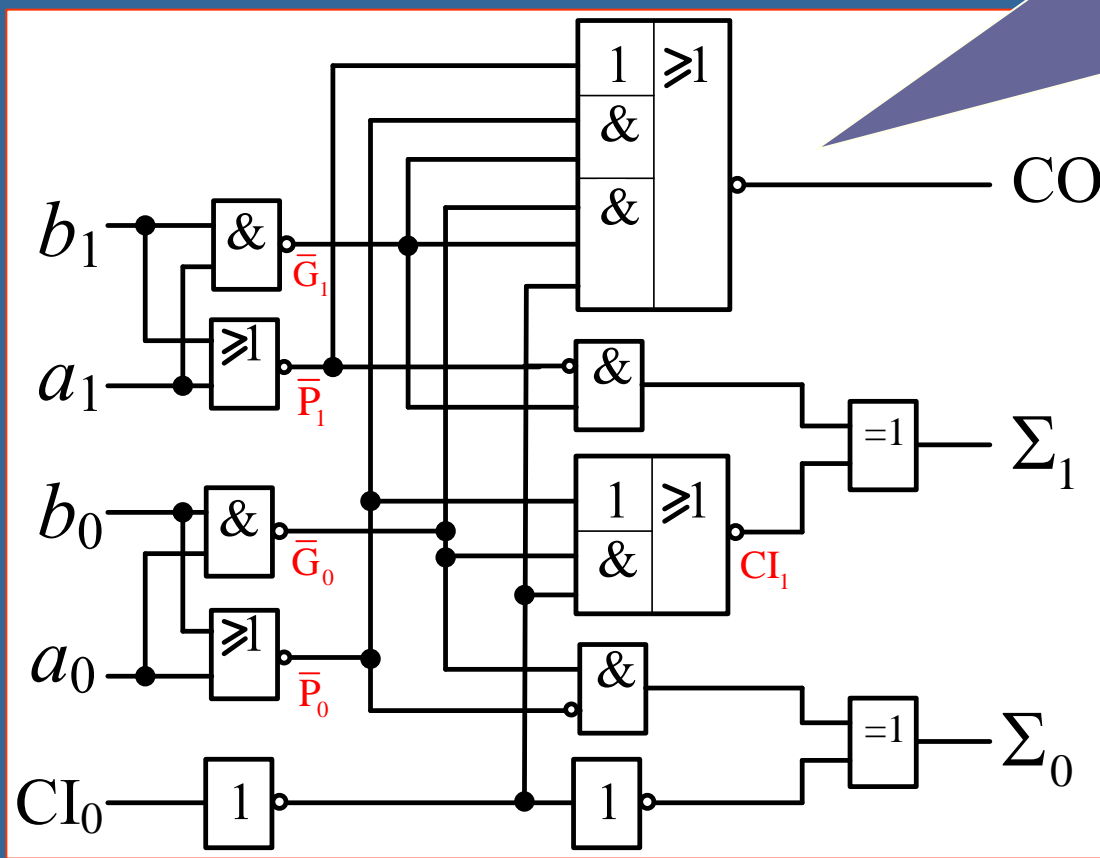


特点：CO由 $a_0$ 、 $b_0$ 、 $a_1$ 、 $b_1$ 和 $CI_0$ 直接产生，不需要 $CI_1$ ，可提高多级加法器的运算速度。

## 常用组合逻辑模块


$CI_i$	$x_i$	$y_i$	$CO_i$	$\Sigma_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

1位全加器

 

什么叫逻辑模块？

例：由1位全加器组成的2位加法器

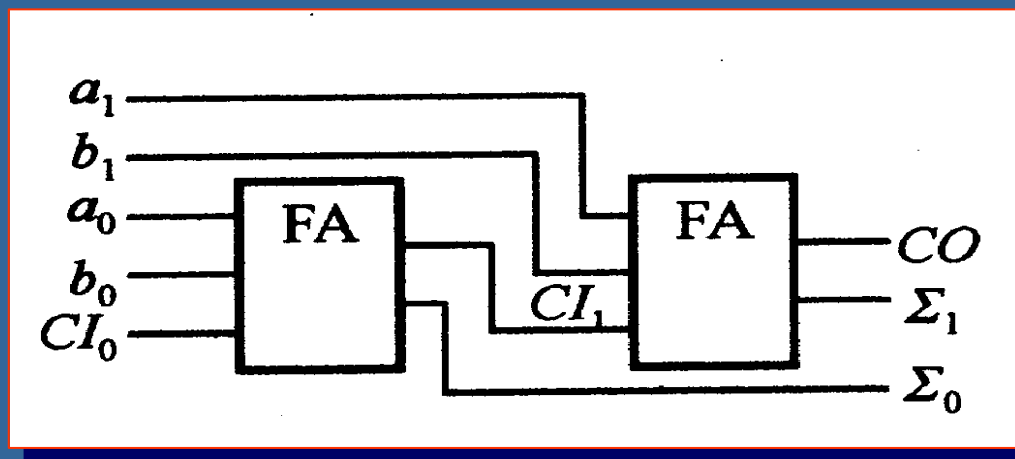

## 逻辑模块化的设计思想

- 1、逻辑设计一般不宜从零开始，而是将现有模块组合修改从而产生新的电路。
- 2、逻辑设计要有清晰的思路，即要非常了解各个模块的性能（本课程之重点就是如何组合各模块）。
- 3、对于具体的模块，可不需过多考虑其内部电路，重点要了解端子上的特性。

# 常用组合 逻辑模块

(教材P108 表3-3-8)

## 中规模集成电路 (MSI)

类 型	类 型		型 号
全加器	2 位二进制		74LS82
	4 位二进制超前进位		74LS83, 74HC283, CD4008B
	BCD 码		CD4560B
数 值 比较器	4 位		74LS85, 74HC85, CD4063B
	8 位		74LS521
	8 位(OC 输出)		74LS522
优 先 编码器	10 线 - 4 线	输出低电平有效	74LS147, 74HC147, 74HCT147
		输出高电平有效	CD40147B
	8 线 - 3 线	输出低电平有效	74LS148, 74HC148
		三态输出低电平有效	74LS348
数 据 选 择 器	8 选 1	同相输出	74LS151, 74HC151, CD4051B
		三态输出	74LS251, 74HC251, 74HCT251
	双 4 选 1	同相输出	74LS153, 74HC153, CD4052B
		三态输出	74LS253, 74HC253, 74HCT253
	四 2 选 1	同相输出	74LS157, 74HC157, 74HCT157
		反相输出	74LS158, 74HC158, 74HCT158
		三态输出	74LS257, 74HC257, 74HCT257
译码器/ 驱动器	4 线 - 16 线	输出低电平有效	74LS154, 74HC154, CD4515B
		输出高电平有效	CD4514B
	3 线 - 8 线	输出低电平有效	74LS138, 74HC138, 74HCT138
		三态输出	74LS538
	双 2 线 - 4 线	输出低电平有效	74LS139, 74HC139, 74HCT139
		三态输出	74LS539
	BCD - 七段码	OC 输出低电平有效	74LS46, 74LS47
		输出高电平有效	CD4055B
		OC 输出高电平有效	74LS49
		输出高电平有效, 内部上拉输出	74LS48
BCD - 十进制 (4 线 - 10 线)	输出低电平有效	74LS42, 74HC42, 74HCT42	
	输出高电平有效, 无驱动	CD4028B	
	三态输出, 无驱动	74LS537	

# 逻辑模块的详细应用资料

## (数值比较器7485)

### SN5485, SN54LS85, SN54S85 SN7485, SN74LS85, SN74S85 4-BIT MAGNITUDE COMPARATORS


SEE 8123 - MARCH 1974 - REVISED MARCH 1985

TYPE	TYPICAL POWER DISSIPATION	TYPICAL DELAY (4-BIT WORMS)
85	275 mW	23 ns
LS85	92 mW	24 ns
S85	285 mW	11 ns

 
#### description

These four-bit magnitude comparators perform comparison of straight binary and straight BCD (8-4-2-1) codes. These fully decoded decisions about two 4-bit words (A, B) are made and are externally available at three outputs. These devices are fully expandable to any number of bits without external gates. Words of greater length may be compared by connecting comparators in cascade. The  $A > B$ ,  $A < B$ , and  $A = B$  outputs of a stage handling less-significant bits are connected to the corresponding  $A > B$ ,  $A < B$ , and  $A = B$  inputs of the next stage handling more-significant bits. The stage handling the least-significant bits must have a high-level voltage applied to its  $A = B$  input. The cascading paths of the '85, 'LS85, and 'S85 are implemented with only a two-gate-level delay to reduce overall comparison times for long words. An alternate method of cascading which further reduces the comparison time is shown in the typical application data.

SN5485, SN54LS85, SN54S85 . . . J OR M PACKAGE  
SN7485 . . . M PACKAGE  
SN74LS85, SN74S85 . . . D OR R PACKAGE



SN54LS85, SN54S85 . . . PK PACKAGE

 

NC: No internal connection.


#### FUNCTION TABLE

COMPARANDS				CASCADING				OUTPUTS			
A3, B3		A2, B2		A1, B1		A0, B0		A = B	A < B	A > B	A = B
A3 > B3	X	X	X	X	X	X	X	X	L	L	L
A3 < B3	X	X	X	X	X	X	X	X	L	L	L
A3 = B3	X	X	X	X	X	X	X	X	L	L	L
A3 > B3	X	X	X	X	X	X	X	X	L	L	L
A3 < B3	X	X	X	X	X	X	X	X	L	L	L
A3 = B3	X	X	X	X	X	X	X	X	L	L	L
A3 > B3	X	X	X	X	X	X	X	X	L	L	L
A3 < B3	X	X	X	X	X	X	X	X	L	L	L
A3 = B3	X	X	X	X	X	X	X	X	L	L	L
A3 > B3	X	X	X	X	X	X	X	X	L	L	L
A3 < B3	X	X	X	X	X	X	X	X	L	L	L
A3 = B3	X	X	X	X	X	X	X	X	L	L	L
A3 > B3	X	X	X	X	X	X	X	X	L	L	L
A3 < B3	X	X	X	X	X	X	X	X	L	L	L
A3 = B3	X	X	X	X	X	X	X	X	L		




# 并行加法器

框图

 

逻辑符号

 


定性符

进位输入

进位输出


# 加法器的级联

## 四位加法器级连成八位加法器

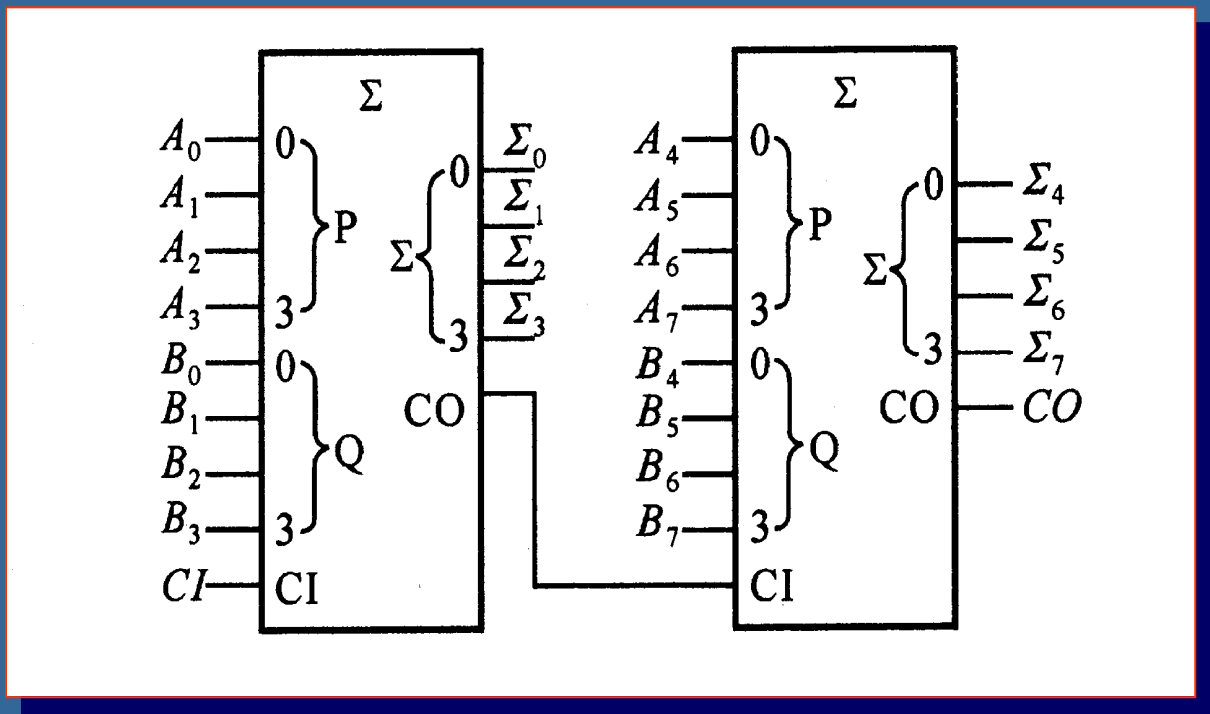

## 加法器的应用 (1)

### 例 1位余3码到1位8421BCD码转换

 


思考：1位8421BCD码转换到1位余3码如何接？

## 加法器的应用 (2)

补充例题 用4位加法器构成1位8421BCD码加法器

1位8421BCD码加法运算规则

 

加法器I: 进行  
二进制加法:  
 $F=A+B$


修正信号产生电路:  
判断是否要修正,  
修正 $C=1$   
 $C=CO_3+C_F>9$

加法器II:  
修正加6,不  
修正加0。

## 加法器的应用 (2)

修正信号产生修正信号C的求解

和数大于9的卡诺图

 

$$C_{F>9} = F_3F_2 + F_3F_1$$


逻辑表达式

$$\begin{aligned} C &= CO_3 + C_{F>9} \\ &= CO_3 + F_3F_2 + F_3F_1 \end{aligned}$$


## 加法器的应用 (2)

修正信号产生电路的实现 (用与或非门74S64)

74S64

 

$$C = CO_3 + F_3F_2 + F_3F_1$$

 

### 与、或门多余输入端的处理方法

- 与门：悬空（CMOS与门除外）、接高电平、与有信号输入端并联。
- 或门：接低电平、与有信号输入端并联。

## 加法器的应用 (2)

### 1位8421BCD码加法器

