
 


SR Latch Latch(SR锁存器)

 - $S = 0, R = 0$: then $Q = Q_{prev}$ and $\bar{Q} = \bar{Q}_{prev}$ (memory!)





- $S = 1, R = 1$: then $Q = 0$ and $\bar{Q} = 0$ (invalid state: $\bar{Q} \neq \text{NOT } Q$)



D Latch(D锁存器)

 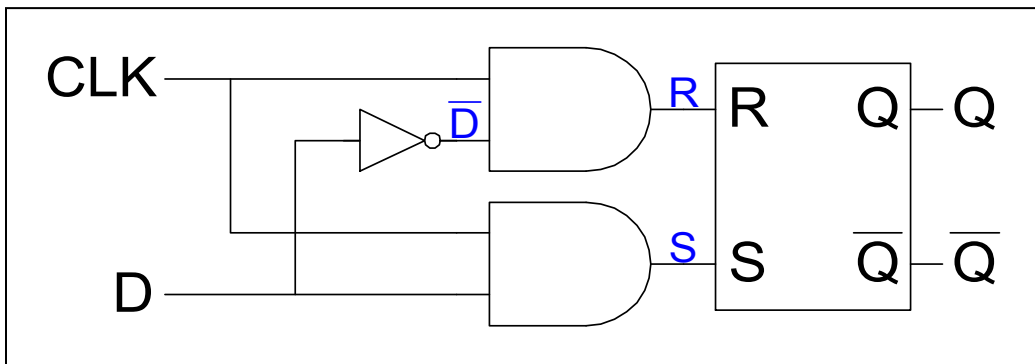锁存器(Latch)是一种对脉冲电平敏感的存储单元电路，它们可以在特定输入脉冲电平作用下改变状态。锁存器的最主要作用是缓存，把信号暂存以维持某种电平状态,其次完成高速的控制器与慢速的外设的不同步问题，再其次是解决驱动的问题，最后是解决一个 I/O 口既能输出也能输入的问题。锁存器是利用电平控制数据的输入，包括不带使能控制的锁存器和带使能控制的锁存器。




CLK	D	\overline{D}	S	R	Q	\overline{Q}
0	X	\overline{X}	0	0	Q_{prev}	\overline{Q}_{prev}
1	0	1	0	1	0	1
1	1	0	1	0	1	0

D Flip-Flop (D触发器)。


- 具有记忆功能, 时钟边沿触发来更新输出数据的
- Two inputs: CLK , D
- *Function*
 - The flip-flop “samples” D on the rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on the rising edge of CLK
- A flip-flop is called an *edge-triggered* (时钟边沿触发) device because it is activated on the clock edge

D Flip-Flop
Symbols

 


D Flip-Flop Internal Circuit

 - Two back-to-back latches (L1 and L2) controlled by complementary clocks
- When $CLK = 0$
 - L1 is transparent
 - L2 is opaque
 - D passes through to N1
- When $CLK = 1$
 - L2 is transparent
 - L1 is opaque
 - N1 passes through to Q
- Thus, on the edge of the clock (when CLK rises from 0→1)
 - D passes through to Q



D Flip-Flop (D触发器)



 
- Two back-to-back latches (L1 and L2) controlled by complementary clocks
- When $CLK = 0$
 - L1 is transparent
 - L2 is opaque
 - D passes through to N1
- When $CLK = 1$
 - L2 is transparent
 - L1 is opaque
 - N1 passes through to Q





在上个时钟结
束时, 数据保
存在这里

在下个时钟沿
到来后, 数据
从这里输出

D Latch vs. D Flip-Flop

   


4-bit Registers (4-位寄存器)

 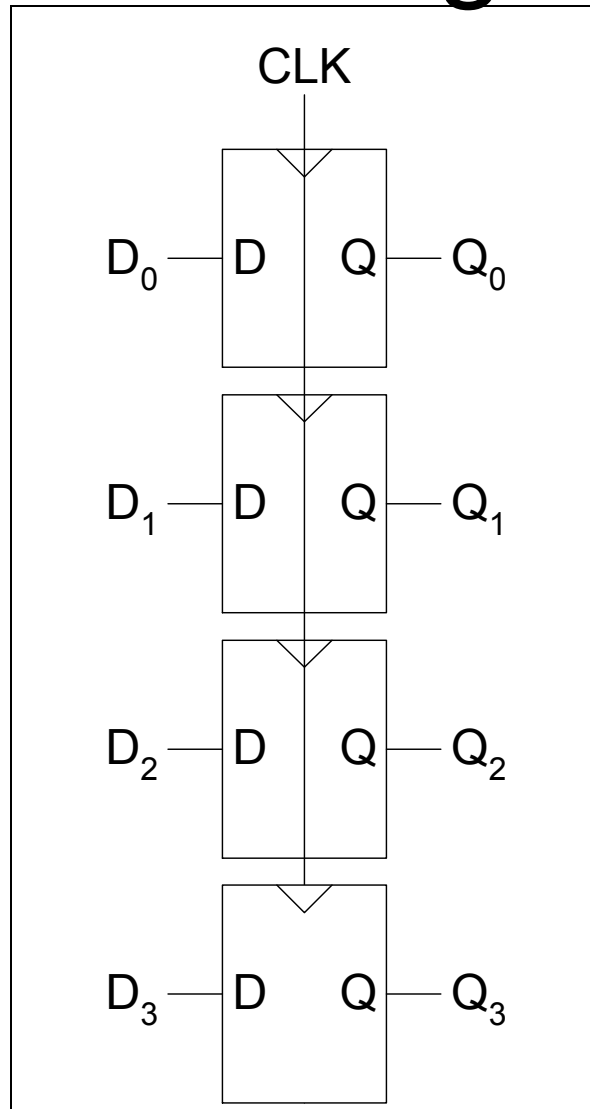

Enabled Flip-Flops

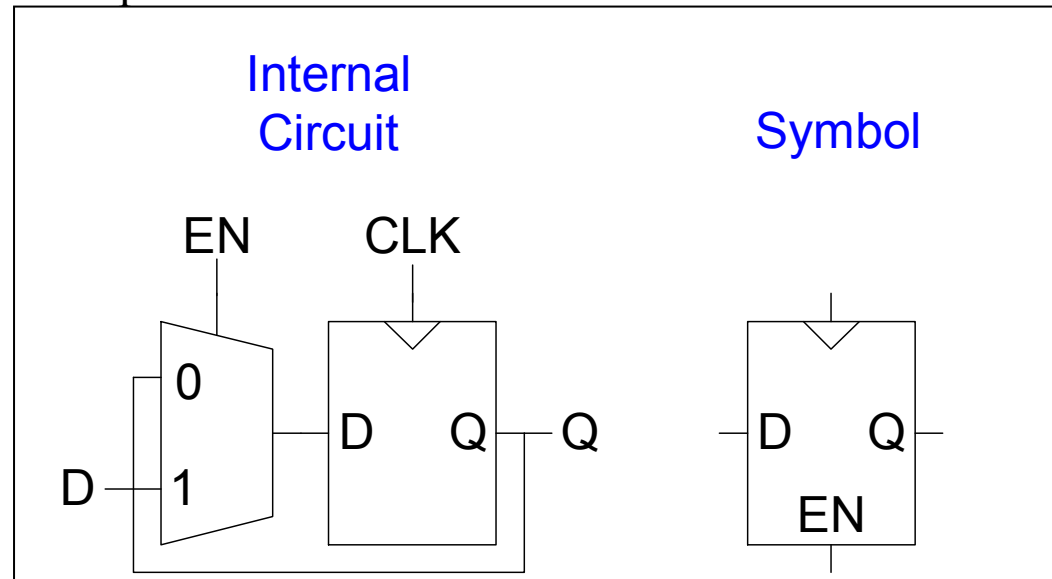
- Inputs: CLK , D , EN
 - The enable input (EN) controls when new data (D) is stored
- Function
 - $EN = 1$
 - D passes through to Q on the clock edge
 - $EN = 0$
 - the flip-flop retains its previous state





Resettable Flip-Flops

- Inputs: CLK , D , $Reset$
- Function:
 - $Reset = 1$ ($\rightarrow \overline{Reset} = 0$)
 - Q is forced to 0
 - $Reset = 0$
 - the flip-flop behaves like an ordinary D flip-flop

Internal
Circuit

 

Symbols

  

Settable Flip-Flops

- Inputs: CLK , D , Set
- Function:
 - $Set = 1$
 - Q is set to 1
 - $Set = 0$
 - the flip-flop behaves like an ordinary D flip-flop

Symbols

